

Assignment

M Shantipriya

CONTENTS

1	Components	1
2	Truth table	2
3	K-MAP	2
4	Procedure	2

QUESTION

For the given boolean expression $f = \bar{a}\bar{b}\bar{c} + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc + ab\bar{c}$, the minimized Product of Sum (POS) expression is

Q(16), GATE/IN-2011

2. The figure given below is the pin diagram of Seven Segment Display.

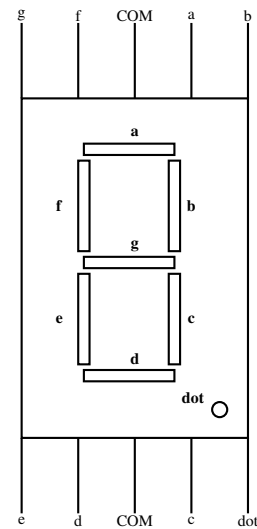


Fig. 1

1 COMPONENTS

Component	Value	Quantity
Resistor	220 Ohm	1
Arduino	UNO	1
Seven Segment Display		1
Decoder	7447	1
Jumper Wires	M-M	20
Breadboard		1

TABLE I

3. The diagram below shows the pin diagram of 7447 BCD Decoder. The output pins of 7447 are connected to Seven Segment Display using Table 2.

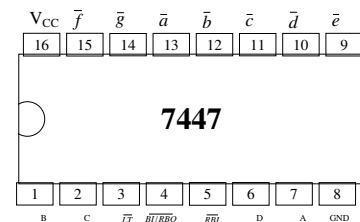


Fig. 2

1. The table given below is the connections between 7447 BCD Decoder and Seven Segment Display

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

TABLE II

2 TRUTHTABLE

a	b	c	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

3 K-MAP

		bc			
		00	01	11	10
a	0	1	0	0	1
	1	1	0	1	1

The minimized expression is $f=(b+\bar{c})(a+\bar{c})$

4 PROCEDURE

1.The given boolean expression is
 $f=\bar{a}\bar{b}\bar{c}+\bar{a}b\bar{c}+a\bar{b}\bar{c}+abc+ab\bar{c}$

from this we can write the minimized POS expression as follows

$$f=\bar{a}\bar{b}\bar{c}+\bar{a}b\bar{c}+a\bar{b}\bar{c}+abc+ab\bar{c}$$

$$f=\bar{a}\bar{c}(\bar{b}+b)+a\bar{c}(\bar{b}+b)+abc$$

$$f=\bar{a}\bar{c}+a\bar{c}+abc$$

$$(\text{additive identity } [\bar{b}+b=1])$$

$$f=\bar{c}(\bar{a}+a)+abc$$

$$f=\bar{c}+abc$$

$$(\text{additive identity } [\bar{a}+a=1])$$

$$f=(\bar{c}+b)(\bar{c}+a)(\bar{c}+c)$$

$$(\text{distributivelaw } A+BC=(A+B)(A+C))$$

$$f=(b+\bar{c})(a+\bar{c})$$

$$(\text{additive identity } [\bar{c}+c=1])$$

2.connect the circuit using 7447 BCD-Seven segment display decoder and Arduino.

3.connect the seven segment pins to 7447 using Table 2.

4.connect the pin A of 7447 to D2 of Arduino and remaining pins B,C and D to GND.

5.connect the pins D4,D5,D6 to 0's and 1's.Change the pins simultaneously to verify the POS expression truth table.

6.Verify the miinimized POS expression operation in arduino using the following code and making pin connections according to fig 2,Table 2

Observe the truthtable and verify the program by executing the link provided below.

<https://github.com/Shantipriya1919/fwc1>