

The minimized POS expression for the given boolean expression through avr-gcc

M Shantipriya

CONTENTS

| | | |
|---|------------|---|
| 1 | Abstract | 1 |
| 2 | Components | 1 |
| 3 | Truthtable | 2 |
| 4 | K-MAP | 2 |
| 5 | Procedure | 2 |

1 ABSTRACT

Abstract—This manual shows how to implement the minimized POS expression for the given boolean expression through avr-gcc.

In the circuit a,b and c are digital inputs, f is digital output. The given boolean expression is $f = \bar{a}\bar{b}\bar{c} + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc + ab\bar{c}$

2 COMPONENTS

| Component | Value | Quantity |
|-----------------------|---------|----------|
| Resistor | 220 Ohm | 1 |
| Arduino | UNO | 1 |
| Seven Segment Display | | 1 |
| Decoder | 7447 | 1 |
| Jumper Wires | M-M | 20 |
| Breadboard | | 1 |

TABLE I

1. The table given below is the connections between 7447 BCD Decoder and Seven Segment Display

| 7447 | \bar{a} | \bar{b} | \bar{c} | \bar{d} | \bar{e} | \bar{f} | \bar{g} |
|---------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|
| Display | a | b | c | d | e | f | g |

TABLE II

2. The figure given below is the pin diagram of Seven Segment Display.

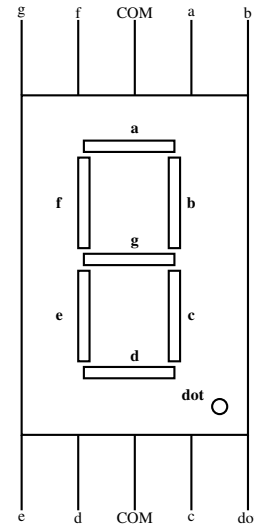


Fig. 1

3. The diagram below shows the pin diagram of 7447 BCD Decoder. The output pins of 7447 are connected to Seven Segment Display using Table 2.

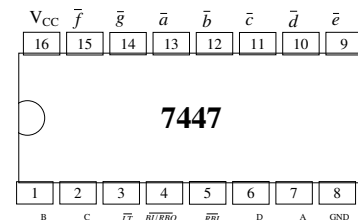


Fig. 2

3 TRUTHTABLE

| a | b | c | f |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

4 K-MAP

| | | | | | |
|---|---|----|----|----|----|
| | | bc | | | |
| | | 00 | 01 | 11 | 10 |
| a | 0 | 1 | 0 | 0 | 1 |
| | 1 | 1 | 0 | 1 | 1 |

The minimized expression is $f=(b+\bar{c})(a+\bar{c})$

5 PROCEDURE

1.The given boolean expression is

$$f=\bar{a}\bar{b}\bar{c}+\bar{a}b\bar{c}+a\bar{b}\bar{c}+abc+ab\bar{c}$$

from this we can write the minimized POS expression as follows

$$f=\bar{a}\bar{b}\bar{c}+\bar{a}b\bar{c}+a\bar{b}\bar{c}+abc+ab\bar{c}$$

$$f=\bar{a}\bar{c}(\bar{b}+b)+a\bar{c}(\bar{b}+b)+abc$$

$$f=\bar{a}\bar{c}+a\bar{c}+abc$$

$$(\text{additive identity } [\bar{b}+b=1])$$

$$f=\bar{c}(\bar{a}+a)+abc$$

$$f=\bar{c}+abc$$

$$(\text{additive identity } [\bar{a}+a=1])$$

$$f=(\bar{c}+b)(\bar{c}+a)(\bar{c}+c)$$

$$(\text{distributivelaw } A+BC=(A+B)(A+C))$$

$$f=(b+\bar{c})(a+\bar{c})$$

$$(\text{additive identity } [\bar{c}+c=1])$$

2.connect the circuit using 7447 BCD-Seven segment display decoder and Arduino.

3.connect the seven segment pins to 7447 using Table 2.

4.connect the pin A of 7447 to D2 of Arduino and remaining pins B,C and D to GND.

5.connect the pins D8,D9,D10 to 0's and 1's.Change the pins simultaneously to verify the POS expression truth table.

6.Verify the miinimized POS expression operation in avr-gcc using the following code and making pin connections according to fig 2,Table 2

Observe the truthtable and verify the program by executing the link provided below.

<https://github.com/Shantipriya1919/fwc1>